 


# Digital Building Blocks



## Arithmetic and Logical Operations using Digital Building Blocks

Chapter 4.1 and 4.2  
“Digital Building Blocks” by R. Verrinder  
EEE2046F/EEE2050F Embedded Systems I notes


  
# Arithmetic and Logical Operations Overview


- Digital processors are used to perform **arithmetic and logical operations**
- Logical circuits can be used to implement these operations
- Arithmetic operations
  - Addition
  - Subtraction
- Logical operations
  - **Comparison**: equality and magnitude comparators
  - **Shifters and rotators**: logical shift, arithmetic shift and rotators



# Arithmetic and Logical Operations
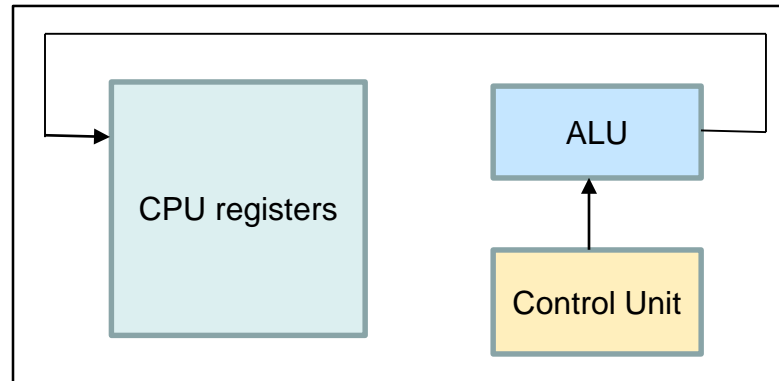
## Design approach: digital circuits

- In digital processors, a **CPU** is responsible for performing the arithmetic and logical operations
- Two approaches to design circuits for n-bit operations
  - **Exhaustive approach**: construct the truth table for all possible inputs and outputs. Then use combinational logic techniques to produce the circuit
  - **Simple, extendable approach**: construct combinational circuits for 2-bit arithmetic and logical operations. Thereafter, extend to n-bit circuits
- The simple, extendable approach is the preferred approach






Simplified block diagram of generic CPU

# Arithmetic and Logical Operations
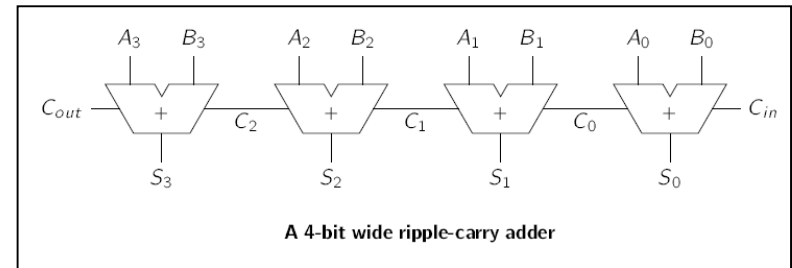  
## Addition: introduction


- **Adders** are used in digital circuits to perform binary addition
- Approach used to design a n-bit adder
  - **1-bit half adder**: a 'carry out' output exists. No 'carry in' input
  - **1-bit full adder**: possess both a 'carry out' and a 'carry in'
  - **Multi-bit adder**: add n-bit binary numbers with a 'carry out' and 'carry in'



# Arithmetic and Logical Operations
 
## Addition: 1-bit half adder

- A 1-bit half adder is a digital circuit used to add two 1-bit numbers:  $A + B$
- Inputs
  - $A$ : a 1-bit binary number
  - $B$ : a 1-bit binary number
- Output
  - $S$ : sum
  - $C_{out}$ : carry out bit




Input		Output	
$A$	$B$	$S$	$C_{out}$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Half Adder truth table

# Arithmetic and Logical Operations
 
## Addition: 1-bit half adder


- The truth table can be used to write out the **logical expression for the outputs**:
  - $S = A \oplus B$
  - $C_{out} = A \cdot B$
- The circuit diagram is made up of an XOR gate and a NAND gate
- **Limitation**: no 'carry in' input bit



# Arithmetic and Logical Operations
 
## Addition: 1-bit full adder

- A 1-bit full adder is a digital circuit used to add two 1-bit numbers,  $A + B$ , while incorporating a 'carry in' bit
- Inputs
  - $A$  : a 1-bit binary number
  - $B$  : a 1-bit binary number
  - $C_{in}$ : a 1-bit carry in bit
- Output
  - $S$  : sum ( $S = A + B + C_{in}$ )
  - $C_{out}$ : carry out bit




Input			Output	
$C_{in}$	$A$	$B$	$S$	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full Adder truth table

# Arithmetic and Logical Operations
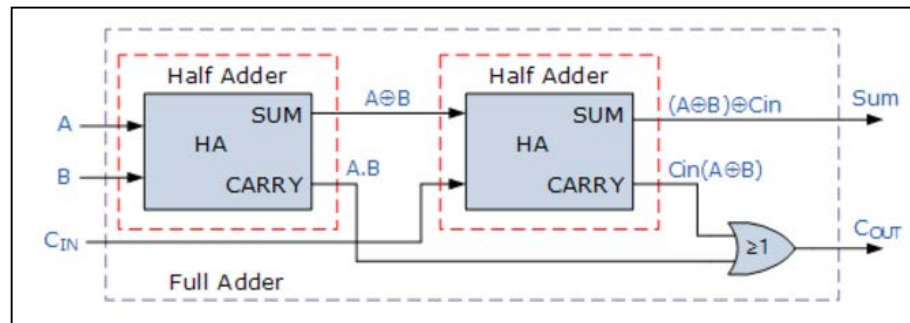
## Addition: 1-bit full adder

- A 1-bit full adder can be constructed by connecting two half adders together




Circuit diagram of a 1-bit full adder (taken from [1])



# Arithmetic and Logical Operations
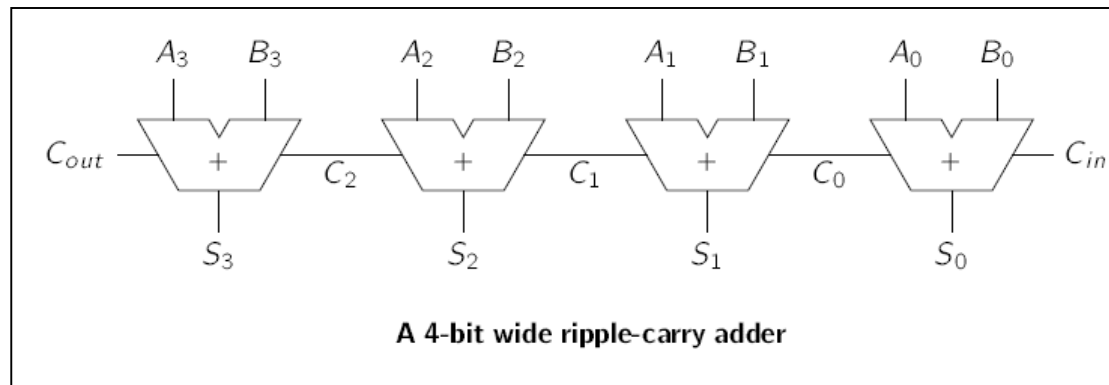
## Addition: n-bit full adder


- A n-bit full adder performs binary addition of **two n-bit numbers**
- This adder architecture is known as a ripple-carry adder
- Properties of a ripple-carry adder
  - Speed =  $n * \text{speed of a 1-bit full adder}$
- Faster adder architecture: carry-look ahead adder



# Arithmetic and Logical Operations
 
## Subtraction: 1-bit half subtractor

- A 1-bit half subtractor is a digital circuit used to subtract two 1-bit numbers, A and B, to output  $D = A - B$
- Inputs
  - A: a 1-bit binary number
  - B: a 1-bit binary number
- Output
  - D: difference output
  - $B_{out}$ : borrow out bit




Input		Output	
A	B	D	$B_{out}$
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Half subtractor truth table

# Arithmetic and Logical Operations
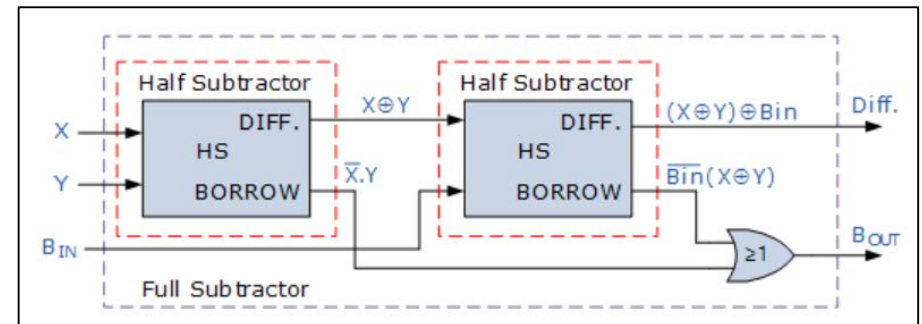
## Subtraction: 1-bit full subtractor

- A 1-bit full subtractor is a digital circuit used to subtract two 1-bit numbers,  $X$  and  $Y$ , while incorporating a 'borrow in' input  $B_{in}$
- Inputs
  - $X$  : a 1-bit binary number
  - $Y$  : a 1-bit binary number
  - $B_{in}$ : a 1-bit borrow in bit
- Output
  - **Diff**: output ( $\text{Diff} = X - Y - B_{in}$ )
  - $B_{out}$ : borrow out bit



Circuit diagram of a 1-bit full subtractor (taken from [2])


# Arithmetic and Logical Operations

## Subtraction: 1-bit full subtractor

- The truth table of a 1-bit full subtractor:  $\text{Diff} = X - Y - B_{\text{in}}$

Truth Table				
B-in	Y	X	Diff.	B-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	1
1	1	1	1	1

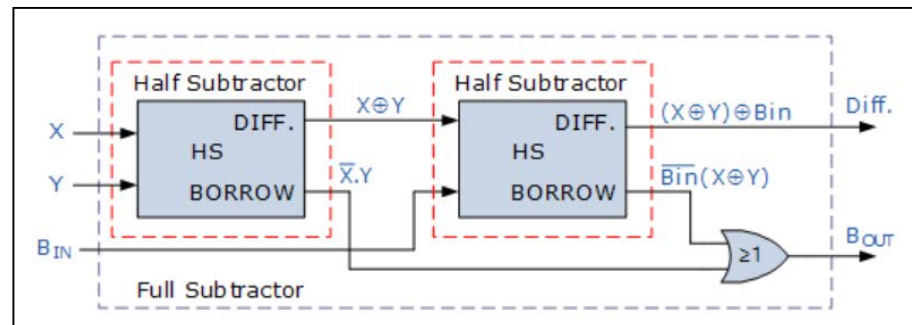Truth table of a 1-bit full subtractor (taken from [2])



Circuit diagram of a 1-bit full subtractor (taken from [2])

# Arithmetic and Logical Operations

## Subtraction: binary numbers

- Subtraction of two binary numbers:  $A - B$
- Another approach to perform subtraction
  - Step 1: find the 2's complement of B, which can be expressed as  $\bar{B} + 1$
  - Step 2: add A and the 2's complement of B:  $A + \bar{B} + 1$

A	B	$A - B$	$\bar{B}$	$A + \bar{B} + 1$
0	0	0	1	0
0	1	1	0	1
1	0	1	1	1
1	1	0	0	0

# Arithmetic and Logical Operations

## Subtraction: binary numbers

- Subtraction of two binary numbers:  $A - B$
- Another approach to perform subtraction
  - Step 1: find the 2's complement of B, which can be expressed as  $\bar{B} + 1$
  - Step 2: add A and the 2's complement of B:  $A + \bar{B} + 1$

A	B	$A - B$	$\bar{B}$	$A + \bar{B} + 1$
0	0	0	1	0
0	1	1	0	1
1	0	1	1	1
1	1	0	0	0


$$\therefore A - B = A + \bar{B} + 1$$

# Arithmetic and Logical Operations

## Subtraction: 1-bit full subtractor

- A 1-bit full adder can be used to perform subtraction:  $A - B$

- $C_{in} = 1$
- Invert B

 

Input		Output	
A	B	D	$B_{out}$
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	1

1-bit subtractor truth table

a '0' represents a borrow from a higher significant bit

a '1' represents a non-borrow from a higher significant bit


- Observe:  $A - B = A + (-B)$   
 $= A + (\overline{B} + 1)$

# Arithmetic and Logical Operations
 
## Subtractor: n-bit full subtractor

- A n-bit full adder can be modified to perform the subtraction of two n-bit binary numbers:  $A - B$
- Use Sel line to configure the circuit to be either a n-bit adder or a n-bit subtractor
  - Sel = 0:  $A + B$
  - Sel = 1:  $A + \overline{B} + 1$

$$\begin{aligned} \text{Sel} \oplus B &= \overline{B} & (\text{Sel} = 0) \\ \text{Sel} \oplus B &= B & (\text{Sel} = 1) \end{aligned}$$







# Arithmetic and Logical Operations
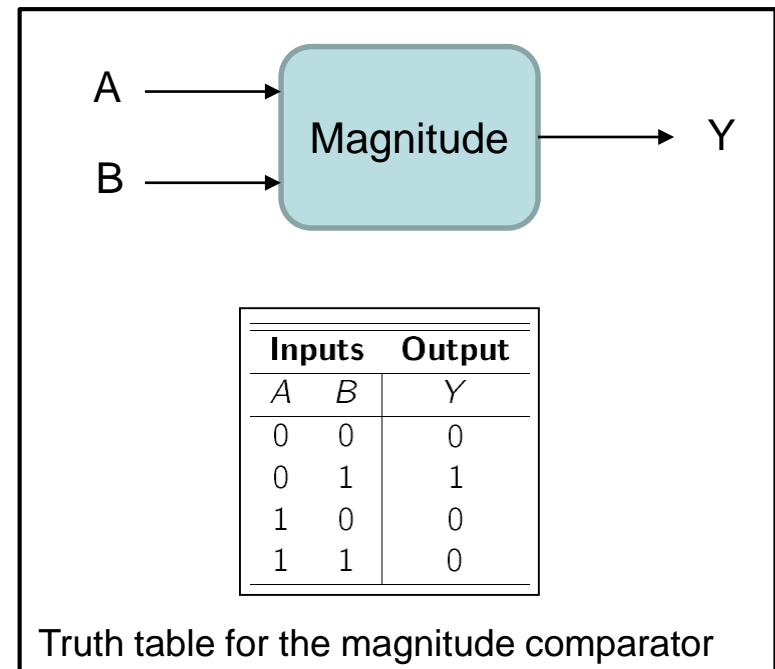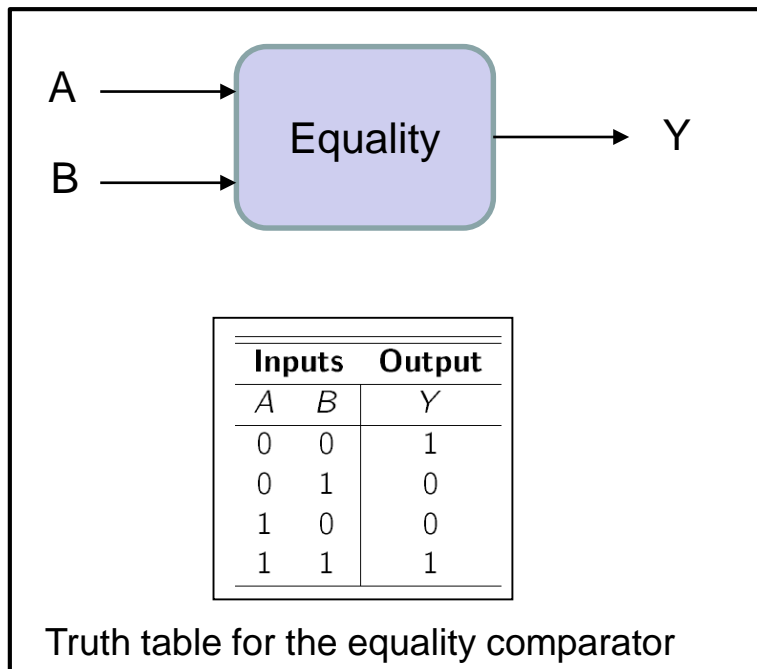
## Comparators: overview

- A comparator is a digital circuit that compares two inputs: A and B.
- Let's look at two types of comparators
  - **Equality comparator**: output Y is HIGH when inputs are equal:  $A == B$
  - **Magnitude comparator**: output Y is HIGH when  $A < B$





# Arithmetic and Logical Operations

## Comparators: equality comparator

- The truth table of a 1-bit equality comparator can be used to write out the **Boolean expression** of the output Y:

$$\begin{aligned} Y &= \bar{A}\bar{B} + AB \\ &= \overline{(A \oplus B)} \end{aligned} \quad \leftarrow \text{XNOR gate}$$

 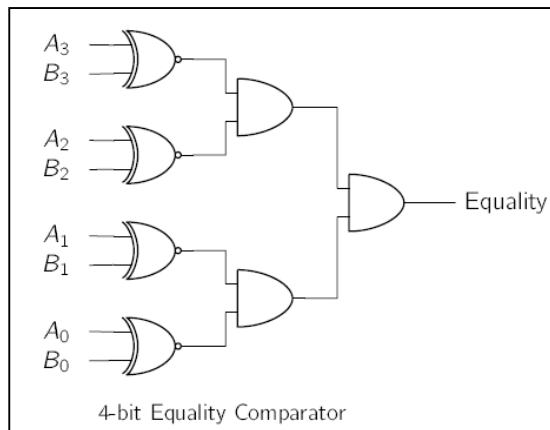
- A n-bit equality comparator is constructed by connecting N 1-bit equality comparators to a multi-input AND gate



# Arithmetic and Logical Operations
 
## Comparators: magnitude comparator

- A magnitude comparator operation can be performed using a subtractor unit:
  - $B_{\text{out}} = 1$ :  $A < B$
  - $B_{\text{out}} = 0$ :  $A \geq B$





Input		Output	
A	B	D	B <sub>out</sub>
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Half subtractor truth table

# Arithmetic and Logical Operations
  
## Shifters and Rotators: overview

- Shifters and rotators are logical operations that **manipulate the position of bits** in a binary string
- The operations shift bits one by one into or out of the MSB or LSB of a binary number
- We will cover **two types of shifters** and rotators:
  - **Logical shift**: used for division and multiplication by 2. Assumes unsigned numbers
  - **Arithmetic shift**: used for division and multiplication by 2. Assumes signed numbers
  - **Rotation**: circular shift operation



# Arithmetic and Logical Operations

## Shifters and Rotators: Logical Shift

- A **logical shift** operation shifts binary bits either to the left or to the right and the empty bits are replaced by zeros
- Example:  $A = 1\ 1\ 1\ 0\ 1\ 0\ 1\ 1$ 
  - Logical 1-bit right shift,  $A \gg 1$  gives  $0\ 1\ 1\ 1\ 0\ 1\ 0\ 1$
  - Logical 1-bit left shift,  $A \ll 1$  gives  $1\ 1\ 0\ 1\ 0\ 1\ 1\ 0$
- A n-bit left logical shift is used for **fast multiplication** by  $2^n$
- A n-bit right logical shift is used for **fast division** by  $2^n$
- Unsigned binary numbers are assumed
- Example
  - Let  $A = 8$ :  $0\ 0\ 0\ 0\ 1\ 0\ 0\ 0$  (decimal value of 8)
  - $A \ll 1$ :  $0\ 0\ 0\ 1\ 0\ 0\ 0\ 0$  (decimal value of 16)  $\times 2$
  - $A \gg 1$ :  $0\ 0\ 0\ 0\ 0\ 1\ 0\ 0$  (decimal value of 4)  $\div 2$

# Arithmetic and Logical Operations

## Shifters and Rotators: Logical Shift



- A 2-bit logical shifter can be constructed using two 1-bit multiplexers

shift = 0

- $Y_1 = A_1$
- $Y_0 = A_0$

shift = 1

- $Y_1 = A_0$
- $Y_0 = 0$

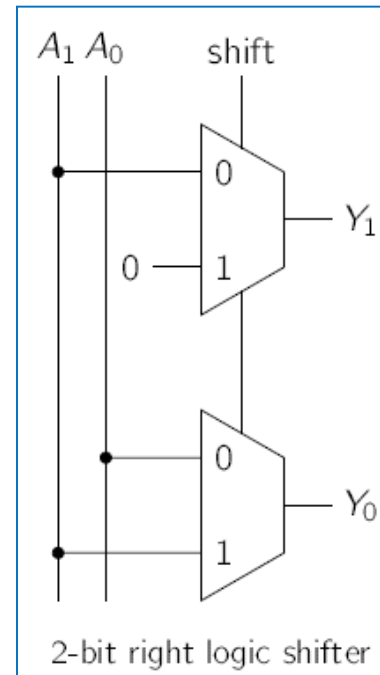 

shift = 0

- $Y_1 = A_1$
- $Y_0 = A_0$

shift = 1

- $Y_1 = 0$
- $Y_0 = A_1$

# Arithmetic and Logical Operations

## Shifters and Rotators: Arithmetic Shift

- There are two types of arithmetic shift operations:
  - **Arithmetic right shift**: bits are shifted to the right and empty bits are replaced by **the original MSB**
  - **Arithmetic left shift**: bits are shifted to the left and empty bits are replaced by **zeros**. An arithmetic left shift is equivalent to a logical left shift
- Example:  $A = 1\ 1\ 1\ 0\ 1\ 0\ 1\ 1$ 
  - Arithmetic 1-bit right shift,  $A \ggg 1$  gives **1 1 1 1 0 1 0 1**
  - Arithmetic 1-bit left shift,  $A \lll 1$  gives **1 1 0 1 0 1 1 0**

# Arithmetic and Logical Operations

## Shifters and Rotators: Arithmetic Shift

- Where are arithmetic shifters used?
- A n-bit right arithmetic shift is used for **fast division** by  $2^n$ 
  - Signed binary numbers are assumed
- A n-bit left arithmetic shift is used for **fast multiplication** by  $2^n$ 
  - Signed binary numbers are assumed
- Example
  - Let  $A = -56$  : 1 1 0 0 1 0 0 0 (decimal value of -56)
  - $A \ggg 1$ : 1 1 1 0 0 1 0 0 (decimal value of -28)  $\div 2$
  - $A \lll 1$ : 1 0 0 1 0 0 0 0 (decimal value of -112)  $\times 2$



# Arithmetic and Logical Operations

## Shifters and Rotators: Arithmetic Shift



- A 2-bit arithmetic shifter can be constructed using two 1-bit multiplexers

shift = 0

- $Y_1 = A_1$
- $Y_0 = A_0$

shift = 1

- $Y_1 = A_0$
- $Y_0 = 0$

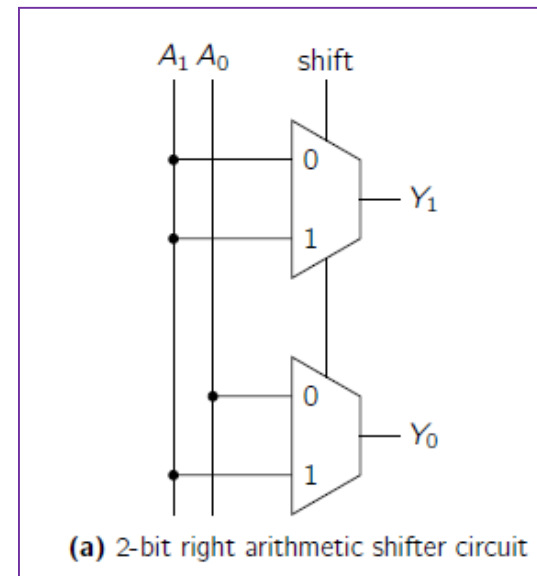 

shift = 0

- $Y_1 = A_1$
- $Y_0 = A_0$

shift = 1

- $Y_1 = A_1$
- $Y_0 = A_1$

2-bit right arithmetic shifter

# Arithmetic and Logical Operations


## Shifters and Rotators: Rotators

- A **rotator** also performs shift operations and empty bits are replaced by the bits that were pushed out
- A rotator performs a **circular shift** operation
- Example
  - Let  $A = 1\ 1\ 1\ 0\ 1\ 0\ 1\ 0$
  - Left rotate  $A: 1\ 1\ 0\ 1\ 0\ 1\ 0\ 1$
  - Right rotate  $A: 0\ 1\ 1\ 1\ 0\ 1\ 0\ 1$

# Arithmetic and Logical Operations
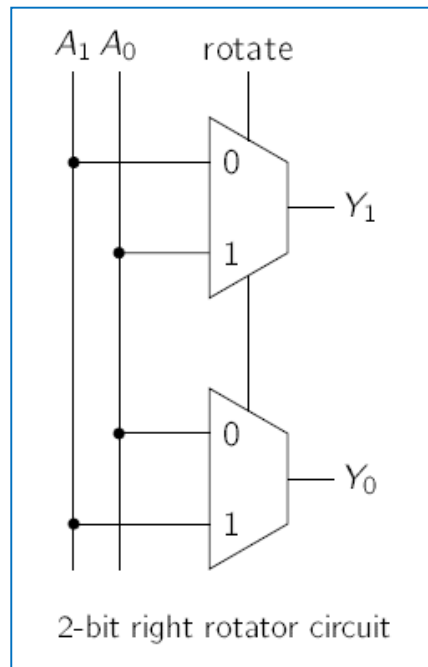
## Shifters and Rotators: Rotators

- A 2-bit rotator can be constructed using two 1-bit multiplexers



shift = 0

- $Y_1 = A_1$
- $Y_0 = A_0$


shift = 1

- $Y_1 = A_0$
- $Y_0 = A_1$

# Arithmetic and Logical Operations
 
## Arithmetic Logic Unit: overview

- An **Arithmetic Logic Unit** (ALU) is the heart of a CPU that is responsible for performing a variety of arithmetic, logical and bit shifting operations
- Inputs
  - **A**: n-bit binary number
  - **B**: n-bit binary number
  - **F**: control bus that specifies the opcode
- Outputs
  - **Y**: n-bit output binary number
  - **S**: status output bits



# Arithmetic and Logical Operations

## Arithmetic Logic Unit: opcodes


- An **opcode** specifies the type of operation that must be done on inputs A and B
- An example of opcode values and operations

Opcode operations.	
Opcode	Operation
000	$A \text{ AND } B$
001	$A \text{ OR } B$
010	$A+B$
011	unused
100	$A \text{ AND } \overline{B}$
101	$A \text{ OR } \overline{B}$
110	$A-B$
111	<b>SET LESS THAN</b> ( $A < B$ )

# Arithmetic and Logical Operations
 
## Arithmetic Logic Unit: status bits


- An **status bits S** provide information about the last output Y
- Typical flags
  - **Carry/Borrow (C)**:
    - For addition,  $X = A + B$ , the C flag is set when there is a carry out of the MSB of the output X. Both A and B are interpreted as unsigned numbers.
    - For subtraction,  $X = A - B$ , the C flag is set when there a borrow from the higher significant bit has not taken place. Both A and B are interpreted as unsigned numbers.
  - **Zero (Z)**: Z is set when the last operation resulted in a zero. Typically used to test equality ( $A == B$ )



# Arithmetic and Logical Operations
 
## Arithmetic Logic Unit: status bits

- Typical flags
  - **Negative or less than (N)**: N is set when the result of the last operation resulted in a negative value or the MSB is set. The result is interpreted as a signed number
    - If the last operation was an addition operation, N is set when the result is greater than  $(2^{n-1} - 1)$  and A and B are n-bit signed numbers
    - If the last operation was a subtraction,  $A - B$ . N is set when  $A < B$ , where both A and B are unsigned numbers
  - **Overflow (V)**: assumes both A and B are n-bit signed numbers and the last operation caused an overflow: outside of the range  $[-(2^{n-1}), (2^{n-1} - 1)]$ . As a result, the 2's complement result of the last output value will be represented incorrectly.



# Arithmetic and Logical Operations

## Arithmetic Logic Unit: Question 1

Design an arithmetic circuit for an ALU with the following instruction set. The opcodes for the instruction set are provided in the table below.

OPCODES AND OPERATIONS			
$F_1$	$F_0$	$C_{in} = 0$	$C_{in} = 1$
0	0	$A$	$A + 1$
0	1	$A + B$	$A + B + 1$
1	0	$A + \bar{B}$	$A - B$
1	1	$A - 1$	$A$

Only design the system for the single-bit per input case. You have the following components available to you: 1-bit wide full adders, 2-to-1 multiplexors, AND, OR, NOT, NOR, NAND and XOR gates, decoders etc.



# Arithmetic and Logical Operations

## Arithmetic Logic Unit: Question 2

Design an arithmetic circuit for an ALU with the following instruction set. The opcodes for the instruction set are provided in the table below.

OPCODES AND OPERATIONS			
$F_1$	$F_0$	$C_{in} = 0$	$C_{in} = 1$
0	0	$A + B$	$A - B$
0	1	$\bar{A} + B$	$B - A$
1	0	$A - 1$	$A + 1$
1	1	$\bar{A}$	$\bar{A} + 1$

Only design the system for the single-bit case. You have the following components available to you: 1-bit full adders, multi-bit wide multiplexors, AND, OR, NOT, NOR, NAND and XOR gates, decoders etc.

# Arithmetic and Logical Operations

## Arithmetic Logic Unit: Question 3

Design an arithmetic circuit for the ALU above, which has a 3-bit instruction set. The opcodes in the instruction set are provided in the table below. Only design the system for the 1-bit case. You have the following components available to you: 1-bit full adders, multi-bit wide multiplexors, AND, OR, NOT, NOR, NAND and XOR gates, decoders etc.

Opcode			Operation
$F_2$	$F_1$	$F_0$	$F$
0	0	0	$A + B$
0	0	1	$A - B$
0	1	0	$\overline{A} + B$
0	1	1	$B - A$
1	0	0	$A - 1$
1	0	1	$A + 1$
1	1	0	$\overline{A}$
1	1	1	$\overline{A} + 1$