

Digital Building Blocks

Registers


Chapter 4.3
“Digital Building Blocks” by R. Verrinder
EEE2046F/EEE2050F Embedded Systems I notes



Registers

Overview

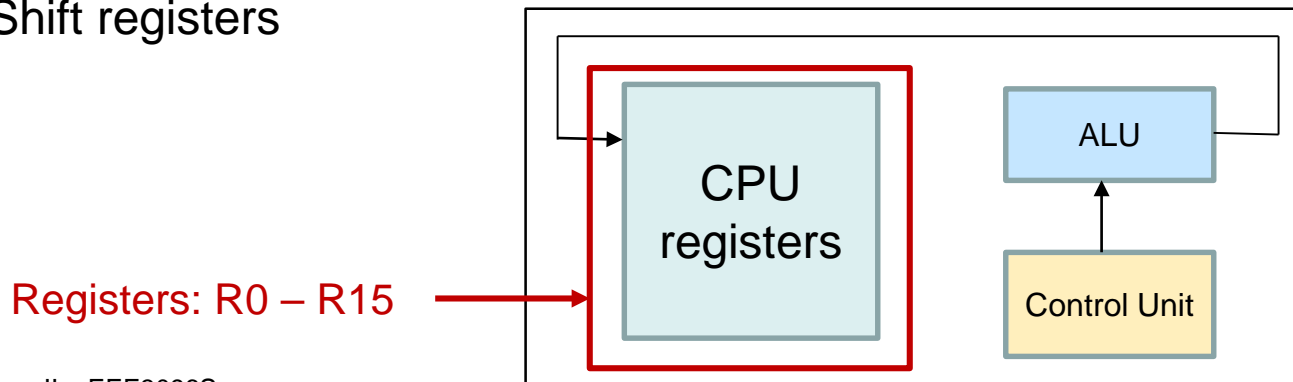
- What is a register?
 - A register is a **memory type** used in a processor
- How are registers used?
 - Registers are used **to store data in binary format**. Thus, a n-bit register can store a n-bit binary number
- Types of registers covered
 - Reset and enable registers
 - Register files
 - Shift registers



Registers

A n-bit register: functionality

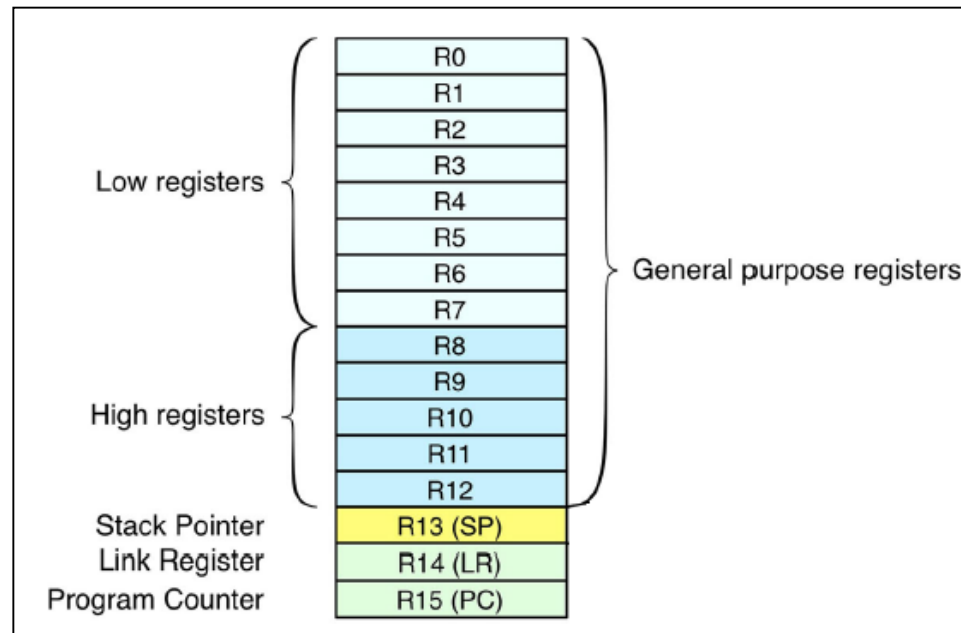
- Functionality of a n-bit register
 - Store n-bits of data
 - Reset n-bits of data
 - Write new n-bits of data into the register



Registers

A practical n-bit register

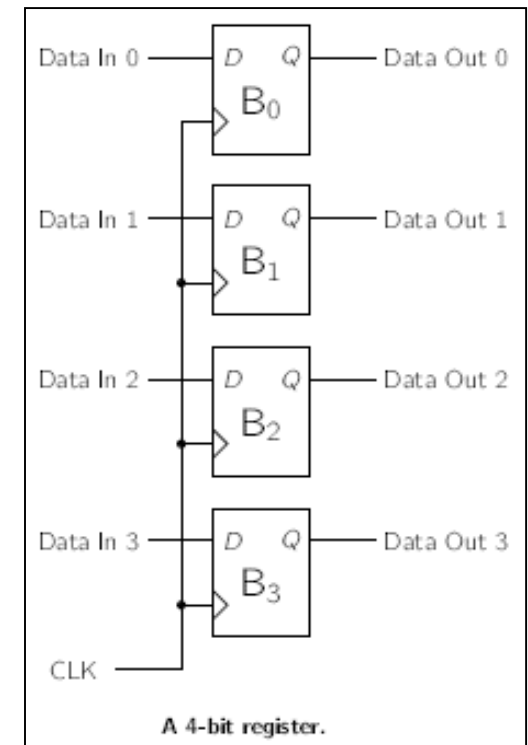- A n-bit register can be constructed using n D flip flops
- Example: a 4 bit register
 - CLK: connects to all flip flops
 - Data input: connects to the D inputs
 - On \uparrow edge of the clock: $Q = D$
 - Data is read from the Q outputs




Registers

Building blocks of a register: D flip flops

- Functionality of a D flip-flop for register usage
 - **Storage**: Q output stores the current output

Operation of a basic D flip flop

D	CLK	Next State of Q
X	0	$Q = Q_{\text{prev}}$
X	1	$Q = Q_{\text{prev}}$

 

D flip-flop symbol


Registers

Building blocks of a register: D flip flops

- Functionality of a D flip-flop for register usage
 - **Storage**: Q output stores the current output
 - **Reset**: R input used to reset $Q = 0$

Operation of a D flip flop with reset

R	D	CLK	Next State of Q
0	X	↑	$Q = D$
1	X	↑	$Q = 0$

 

D flip-flop with reset symbol

Registers


Building blocks of a register: D flip flops

- Functionality of a D flip-flop for register usage
 - **Storage**: Q output stores the current output
 - **Reset**: R input used to reset $Q = 0$
 - **Write**: Enable (En) used to load input data to the output
 - $En = 0$, $Q = Q_{prev}$ on \uparrow CLK
 - $En = 1$, $Q = D$ on \uparrow CLK

Operation of a D flip flop with enable

En	R	D	CLK	Next State of Q
0	0	X	\uparrow	$Q = Q_{prev}$
1	0	X	\uparrow	$Q = D$

 \uparrow represents the rising edge of the clock




D flip-flop with reset and enable

Registers

A practical n-bit register with reset and enable

- A n-bit register with reset and enable functionality can be constructed using n D flip-flops with R and En pins
- Example: a 4-bit register with reset and write enable
 - **Storage**: current outputs are stored in Q
 - **Reset**: $R = 1$ sets $Q = 0$
 - **Write**: $En = 1$ activates D flip flop.
On \uparrow CLK, $Q = D_{in}$
 - **Disable write**: $En = 0$ deactivates D flip flops.
On \uparrow CLK, $Q = Q_{prev}$

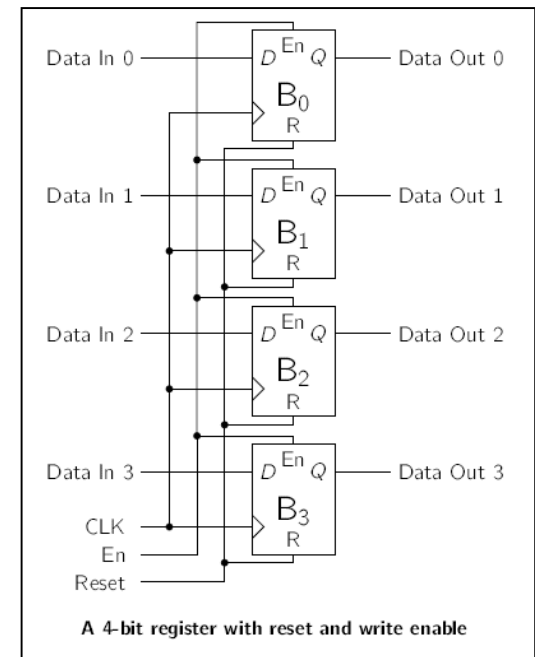


Register Files



Register Files

Introduction

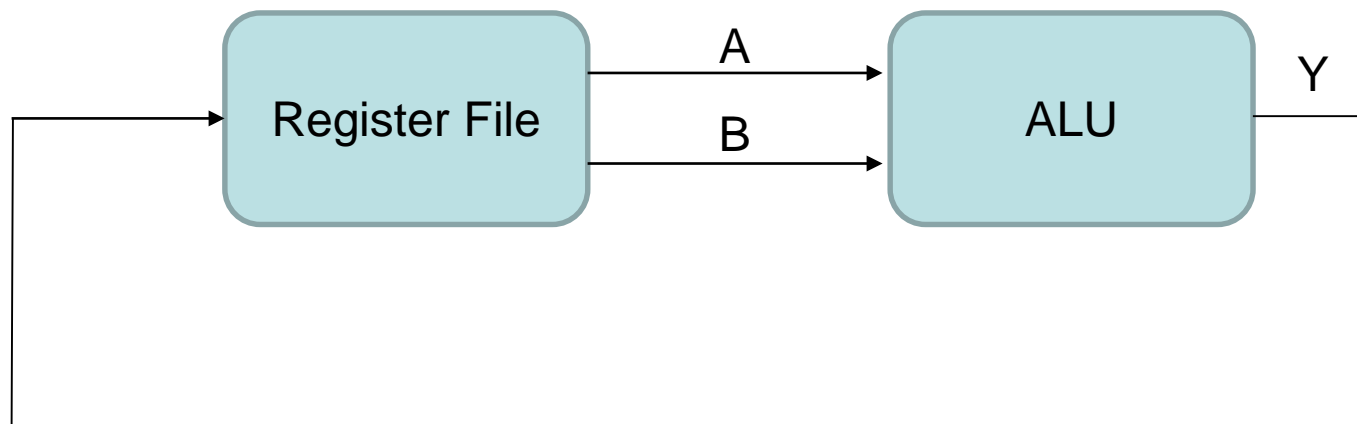
- A register file is a **basic memory structure** that is used in a CPU to perform the following functionality:
 - **Output the values** A and B that are inputs to the ALU
 - **Store** the output Y from the ALU
- The registers are typically as wide as the word length of the CPU and used as a temporary storage structure



Register Files

A 4-bit register file

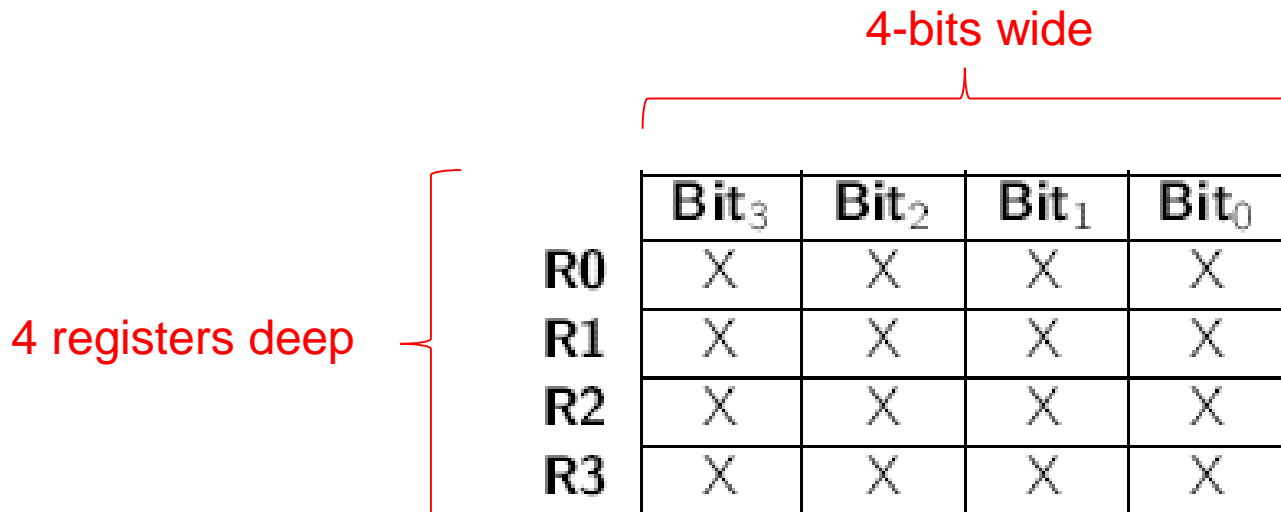
- Let's look at an example of a **4-bit register file** to understand its functionality
- Properties** of a 4-bit register file
 - 4 registers deep,
 - Each register is 4 bit wide



Register Files

A 4-bit register file: functionality

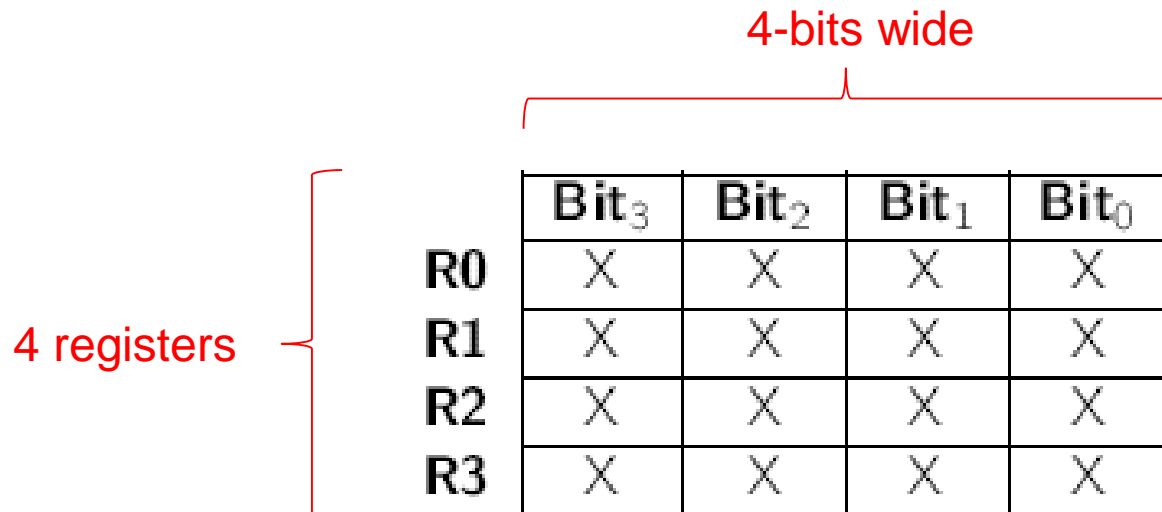- A register file has the following **functionality**:
 - Read
 - Reset
 - Write
 - Disable write




Register Files

A 4-bit register file: read functionality

- **Two outputs**, A and B, can be read out of the register file using the following steps
 1. Set the 2-bit read address for A on RDAddrA
 2. Set the 2-bit read address for B on RDAddrB
 3. Ensure that Reset is cleared: $R = 0$
 4. On the next \uparrow of the CLK, DataOutA and DataOutB will have the contents of the registers at addresses RDAddrA & RDAddrB respectively


Address		Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

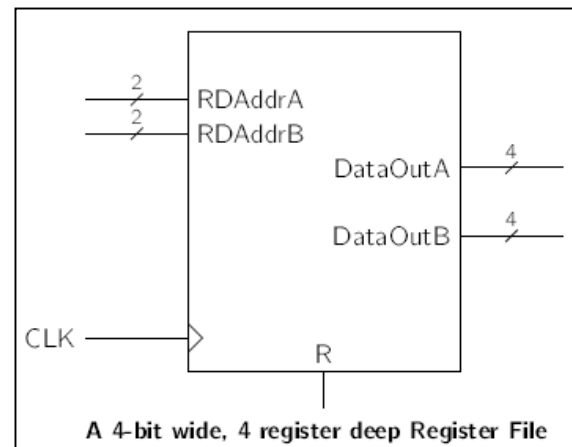

Register Files

A 4-bit register file: reset functionality

 - All four registers can be **reset** using the following steps:
 1. Ensure that Rest is set: $R = 1$
 2. On the next \uparrow of the CLK, all 4 registers will have the binary value '0000'




Register Files

A 4-bit register file: write functionality

- A four-bit binary value can be written to one of the four registers in the following way:
 1. Set the 2-bit write address on WRAddr
 2. Let DataIn = 4 bit binary value to be written
 3. Set WriteEn = 1, and ensure R = 0
 4. On the next \uparrow of the CLK, the register contents specified by WRAddr will contain the 4-bit binary value

Address		Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

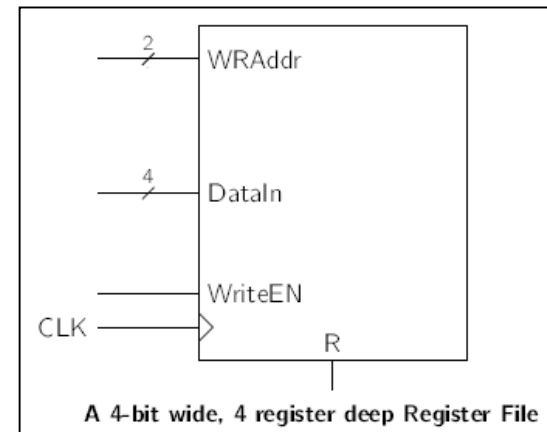


Register Files

A 4-bit register file: disable write functionality

- The write functionality is disabled in the following way:
 - Set **WriteEn** = 0, and ensure $R = 0$
 - On the next \uparrow of the CLK, the register contents of the register file, R0 – R4, will remain the same

Address		Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

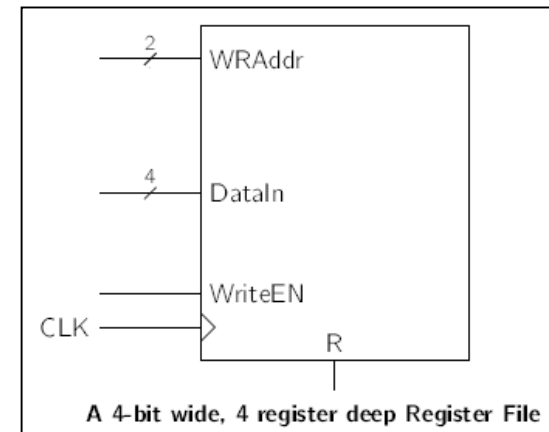


Register Files

A 4-bit register file: all functionality

- A register file with all its functionality:
 1. **Read:** RDAddrW, RDAddrB, DataOutA, DataOutB,
 2. **Reset:** R
 3. **Write:** WRAddr, DataIn, WriteEn
 4. **Disable write:** WriteEn

Address		Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

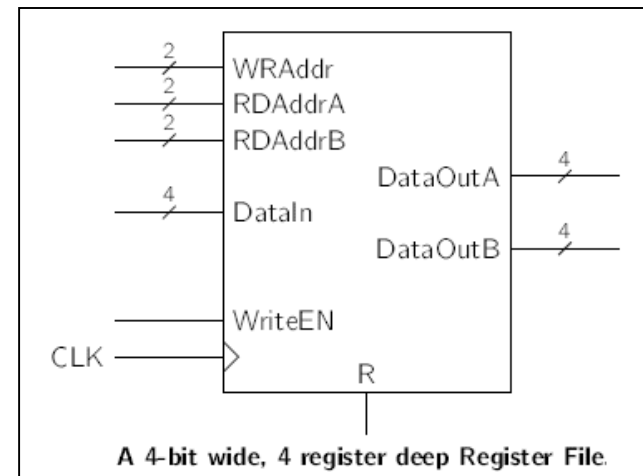



Shift registers



Shift Registers

Overview

  
- Shift registers are specialized registers used to **convert data from one format to another**
- Three types covered
 - Serial in/ serial out
 - Serial in/ parallel out
 - Parallel in/ serial out
- Why are shift registers important?
 - They are used in **low-level communication interfaces** in microcontrollers to shift data into or out of a device



Shift Registers

Serial versus parallel interface

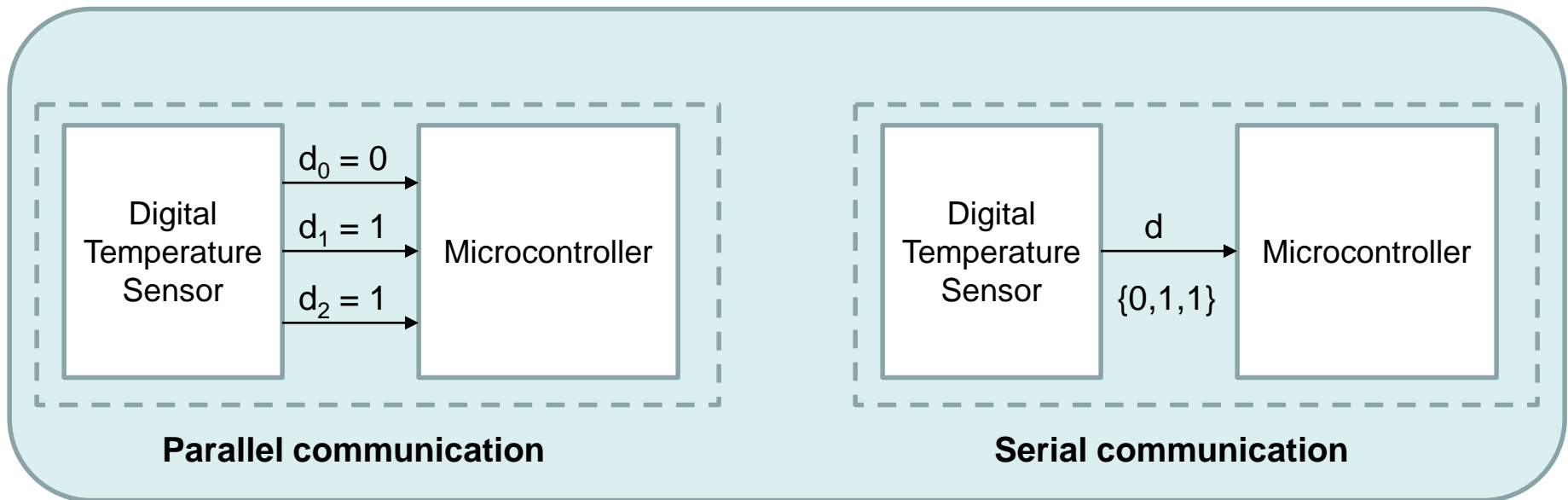
- In a parallel interface, n-bits of data are transferred **at the same time**
- In a serial interface, n-bits of data are **transferred one bit at a time**



Shift Registers

Serial in/ serial out

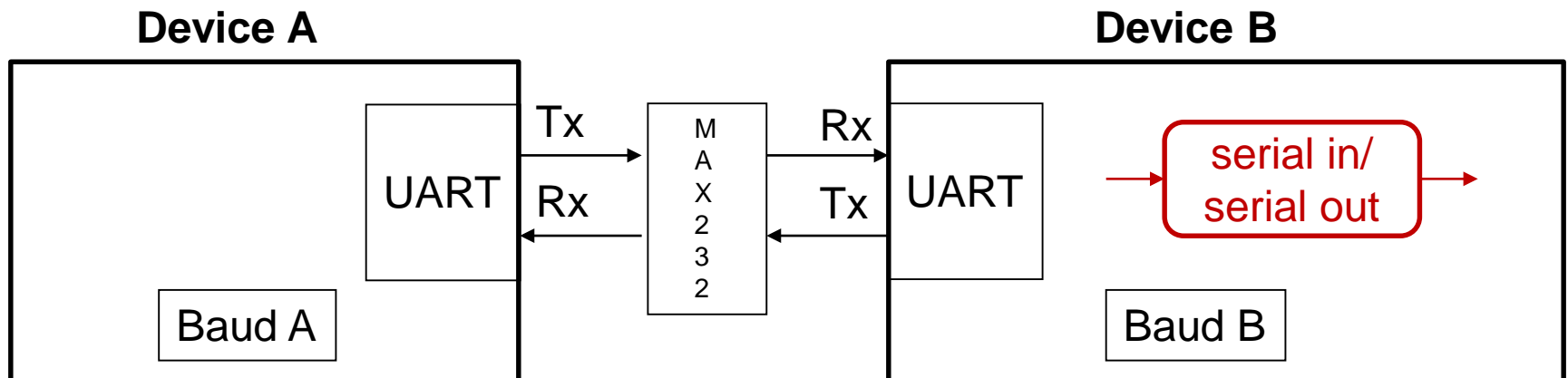
- A serial in/ serial out shift register takes in n-bits of asynchronous serial data and **outputs n-bits of synchronous serial data**
- Example:
 - Device A exchanges serial data with device B asynchronously
 - Device B may use a serial in/ serial out register to **convert an asynchronous serial data into a synchronous serial data**



Shift Registers

Serial in/ serial out

 - A n-bit serial in/ serial out shift register is made up of **n D flip flops**
- An output of a flip flop is fed into the input of the next flip flop
- On the \uparrow of the CLK, data is shifted through the register



Shift Registers

Serial in/ serial out: principle of operation

- Example: a 4-bit serial in/ serial out shift register
 - Consider a binary value of **1010** as the input
 - After every \uparrow of the CLK, a new bit is shifted into the register
 - It takes 4 clock cycles for the first bit of the serial message to appear on the output


CLK	Q ₀	Q ₁	Q ₂	Q ₃	Output
0	0	0	0	0	
1	0	0	0	0	0
2	1	0	0	0	00
3	0	1	0	0	000
4	1	0	1	0	0000
5	0	1	0	1	00000
6	0	0	1	0	100000
7	0	0	0	1	0100000
8	0	0	0	0	10100000

The operation of a 4-bit Serial In/Serial Out Shift Register

Shift Registers

Serial in/ parallel out

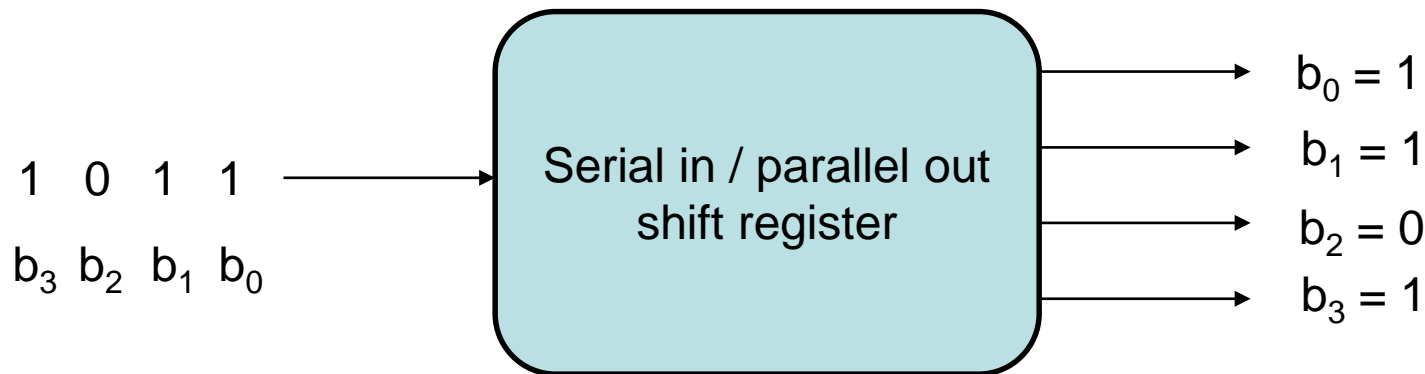
- A serial in/ parallel out shift register takes a n-bit serial number and converts it into a n-bit parallel interface



Shift Registers

Serial in/ parallel out

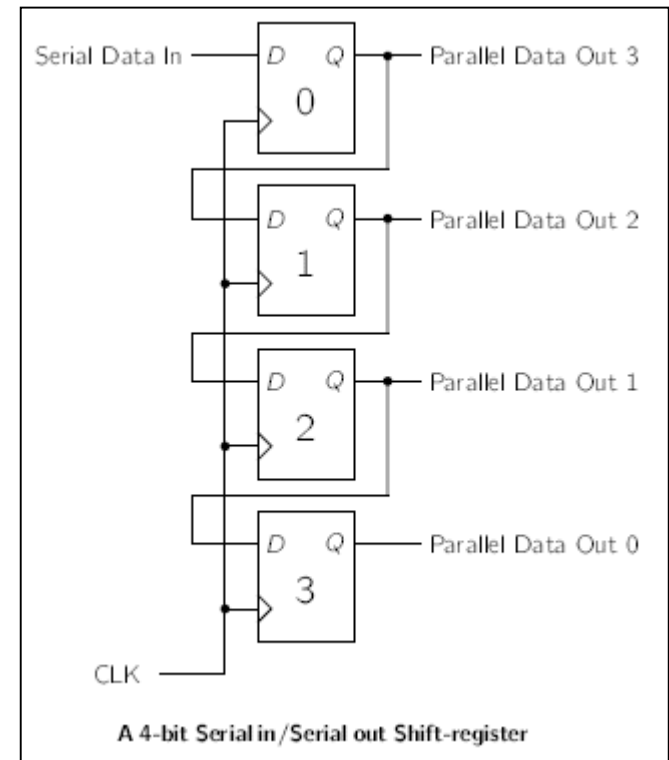- Example: the circuit diagram for a 4-bit serial in/ parallel out shift register is made up of 4 flip flops
- It is similar to a serial in/ serial out shift register, where the data outputs are the Q outputs of the flip flops
- It is used to convert a serial input stream of binary data into a multiple wire parallel output within a embedded system



Shift Registers

Serial in/ parallel out

- Example: a 4-bit serial in/ parallel out shift register showing the **principle of operation**
 - Consider a binary value of **1010** as the input
 - After every \uparrow of the CLK, a new bit is shifted into the register
 - It takes 4 clock cycles for the full binary value to be present on the four Q outputs

CLK	Q ₀	Q ₁	Q ₂	Q ₃	Output
0	0	0	0	0	0000
1	0	0	0	0	0000
2	1	0	0	0	1000
3	0	1	0	0	0100
4	1	0	1	0	1010

The operation of a 4-bit Serial In/Parallel Out Shift Register

Questions

Register operations

Given two 2-bit registers (R0 and R1) (both registers have reset and enable pins), design a circuit which will implement the following register transfer operations. These operations synchronously transfer data between the registers based on a binary opcodes. A table of the opcodes and their transfer operation is given below.

Opcode		Operation	
F_1	F_0	Function	
0	0	F0	$R1 \leftarrow 0$
0	1	F1	$R1 \leftarrow \overline{R1}$
1	0	F2	$R0 \leftarrow \overline{R0}$
1	1	F3	$R1 \leftarrow R0$

- F0: $R1 \leftarrow 0$ (Clear R1 synchronously with the clock signal)
- F1: $R1 \leftarrow \overline{R1}$ (Complement R1)
- F2: $R0 \leftarrow \overline{R0}$ (Complement R0)
- F3: $R1 \leftarrow R0$ (Copy contents of R0 to R1)